

**Lab Work: Experiment-5: Verification of Maximum Power Transfer Theorem**

\*\*\*\*\*

## Verification of Maximum Power Transfer Theorem

### 6.1 Purpose/Objective:

The aim of this experiment is-


- To be familiar with the Maximum Power Transfer theorem and also to verify it.
- To know about its applicability.

### 6.2 Theory:

- Maximum power transfer theorem may be stated as follows:
  - A resistive load will receive maximum power from a network when the load resistance is equal to the Thevenin resistance of the network applied to the load. That is, when

$$R_L = R_{Th}$$

- But, if the load resistance is lower or higher in value than the Thevenin resistance of the network, its dissipated power will be less than the maximum.
- Let us consider the Thevenin's equivalent circuit given below where  $R_2$  is designated as the "load" resistor. We apply Maximum Power Transfer Theorem on this circuit:

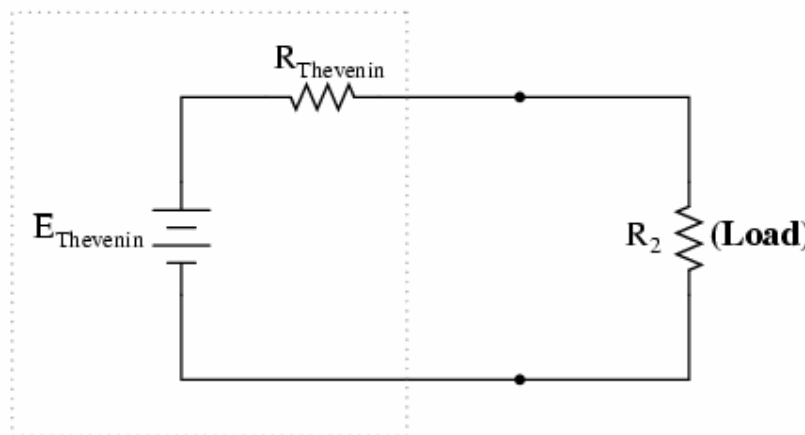

**Figure-1: Thevenin equivalent Circuit**

\*\*\*\*\*

**Lab Work: Experiment-5: Verification of Maximum Power Transfer Theorem**

\*\*\*\*\*

**6.3 Equipment/ Apparatus:**

- a) One regulated variable Power Supply (0-30 V)
- b) Ammeter and voltmeter
- c) Circuit Experiment Board (Breadboard)
- d) Fixed and variable resistors
- e) Connecting wires
- f) Cutting tools etc.


**6.4 Cautions:**

- 1. All connections should be tight and correct.
- 2. Switch off the supply when not in use.
- 3. Reading should be taken carefully.

**6.5 Circuit Diagram:**

The following Thevenin's equivalent circuit is chosen to verify Maximum Power Transfer theorem.

*Thevenin Equivalent Circuit*

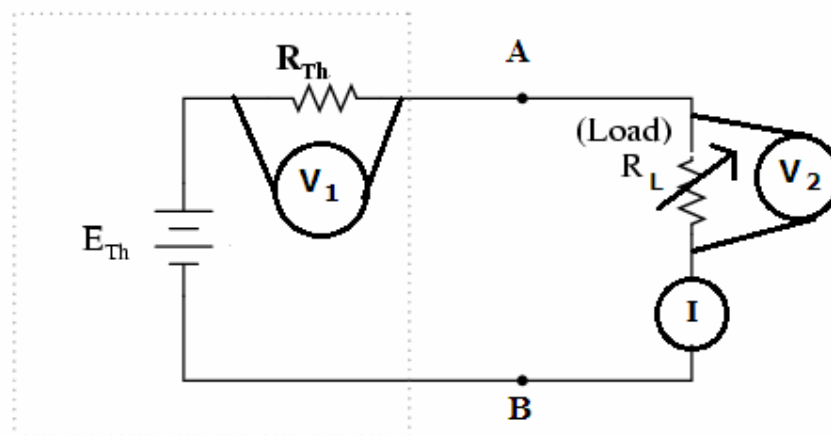

**Figure-2: Thevenin's equivalent of a circuit with variable load resistor**


\*\*\*\*\*



**Lab Work: Experiment-5: Verification of Maximum Power Transfer Theorem**

\*\*\*\*\*


- The PL-RL graph of maximum power transfer theorem should look like this:

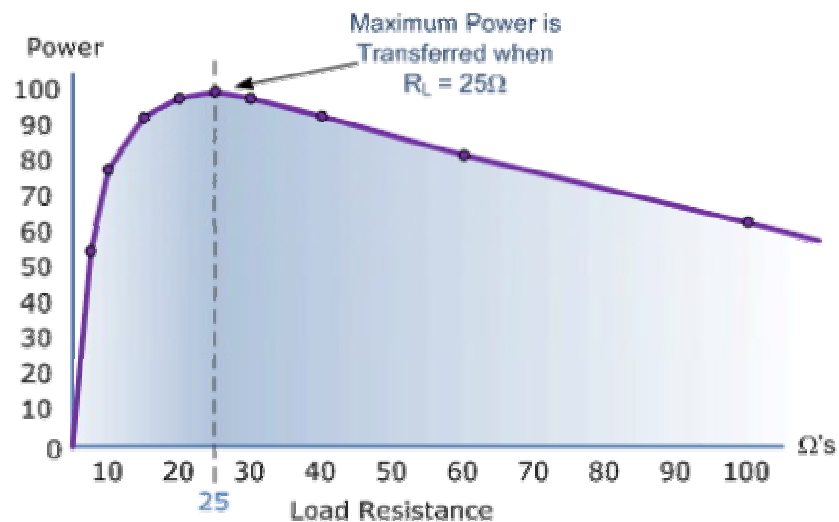

**Figure-3: Graph of Power against Load Resistance**

- From the above graph we can see that the **Maximum Power Transfer** occurs in the load when the load resistance,  $R_L$  is equal in value to the Thevenin's equivalent resistance,  $R_{Th}$ , so then:

\*\*\*\*\*

**Lab Work: Experiment-5: Verification of Maximum Power Transfer Theorem**

\*\*\*\*\*

\*\*\*\*\*