

**Lab Work: Experiment-6: Verification of Norton's Theorem**

\*\*\*\*\*

## Verification of Norton's Theorem


### 5.1 Purpose/Objective:

The aim of this experiment is-

- To be familiar with the Norton's theorem and also to verify it.
- To know about its applicability.

### 5.2 Theory:

- **Norton's Theorem** states that "any linear bilateral circuit containing several energy sources and resistances can be replaced by a single constant current source  $I_{Norton}$  in parallel with a single resistor  $R_{Norton}$ " which is connected in parallel to a load resistor  $R_L$  where the value of the current source ( $I_{Norton}$ ) is the short circuit current between the two terminals of the network and the resistance ( $R_{Norton}$ ) is equal to the equivalent resistance measured between the terminals with all the energy sources eliminated.
- The voltage sources are eliminated by shorting their terminals and the current sources are eliminated by opening their terminals.
- The Norton's equivalent network looks like this:

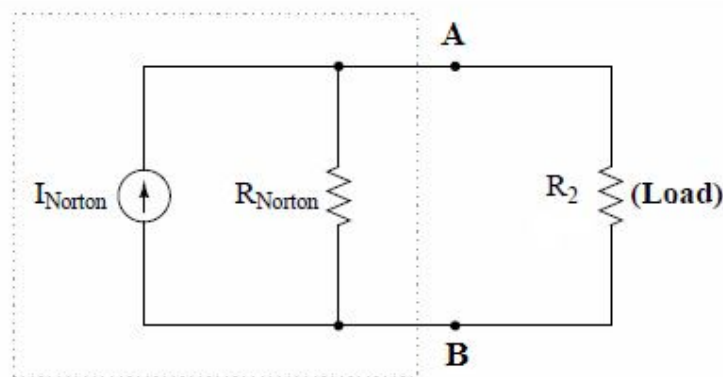

**Figure-1: Norton's equivalent Circuit**

- Consider the circuit given below where  $R_2$  is designated as the "load" resistor. We apply Norton's Theorem to it:

\*\*\*\*\*

Lab Work: Experiment-6: Verification of Norton's Theorem

\*\*\*\*\*

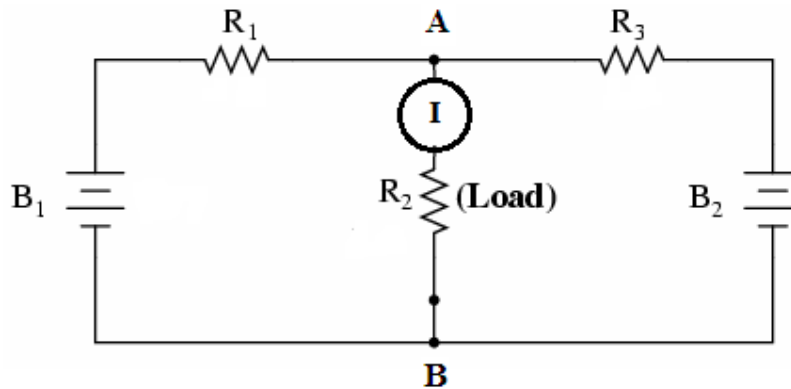


Figure-2: The original circuit under test

In the above circuit,  $I$  represent the value of current through the load resistor  $R_2$ . We want to find this current using Norton's theorem.

- To find the current  $I$  through the load resistor  $R_2$ , just follow the steps below:
  1. Remove the load resistor  $R_2$  between terminal A and B and connect an ammeter between these terminals. Now the circuit looks like this:

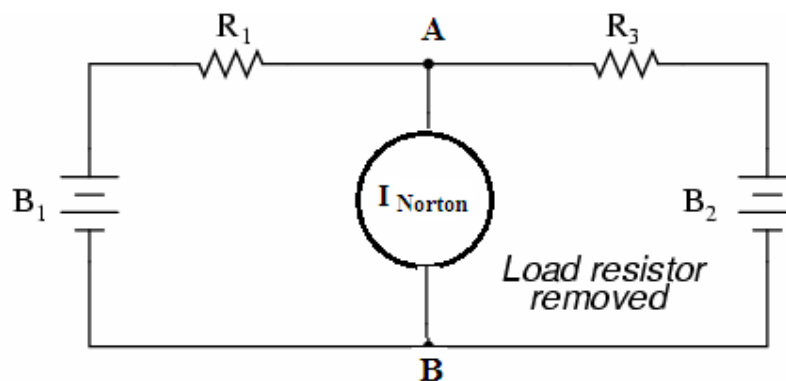



Figure-3: Calculating  $I_{Norton}$  by removing load resistor  $R_2$

2. Determine Norton's current  $I_{Norton}$  by the above circuit.
3. Now determine the Norton resistance  $R_{Norton}$  by removing load resistor from terminal A and B, and removing the power sources and then shorting their terminals as shown in the figure below:

\*\*\*\*\*

**Lab Work: Experiment-6: Verification of Norton's Theorem**


\*\*\*\*\*

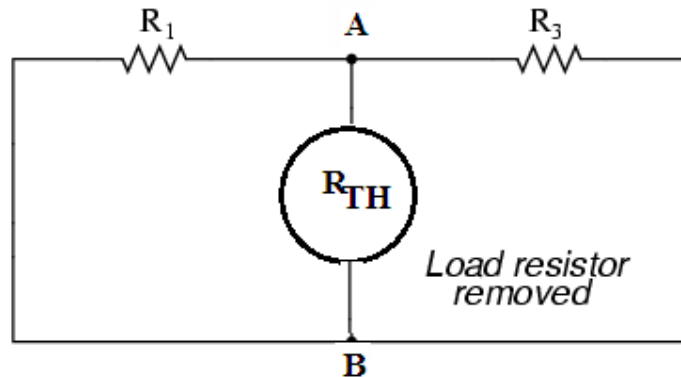

*voltage sources are  
eliminated by shorting  
their terminals*

**Figure-4: Calculating  $R_{Norton}$**

4. After determining the value of  $I_{Norton}$  and  $R_{Norton}$ , the Norton's equivalent circuit is constructed and load resistor  $R_2$  is attached between the terminal A and B shown below:

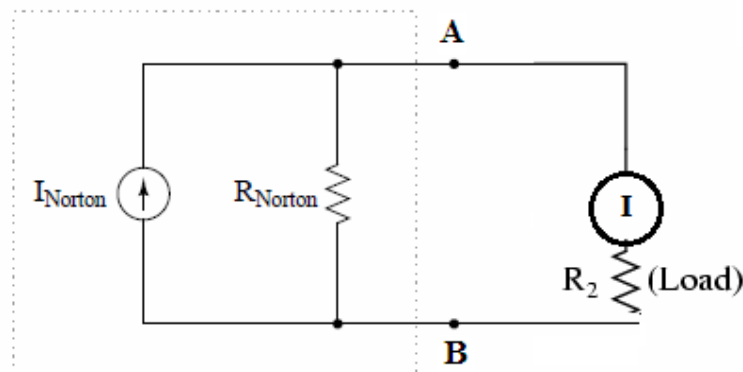

**Figure-5: Norton's equivalent circuit with load resistor reattached**

- If the current reading of figure-2 is same as the reading found in figure-5, then Norton's theorem will be verified.

**5.3 Equipment/ Apparatus:**

\*\*\*\*\*

**Lab Work: Experiment-6: Verification of Norton's Theorem**

\*\*\*\*\*

- a) Two regulated variable Power Supply (0-30 V)
- b) One constant current source
- c) One Digital Multimeter
- d) Circuit Experiment Board (Breadboard)
- e) Three resistors
- f) Connecting wires
- g) Cutting tools etc.

**5.4 Cautions:**

1. All connections should be tight and correct.
2. Switch off the supply when not in use.
3. Reading should be taken carefully.

**5.5 Circuit Diagram:**

The circuit diagrams to verify Norton's theorem are shown in figure-2, figure-3, figure-4 and figure-5 above.

**5.6 Procedure:**

1. Construct the circuit on the breadboard, as shown in figure-2 and observe the voltage of the two sources  $B_1$  and  $B_2$ . Now take the ammeter reading  $I$ .
2. Remove the load resistor  $R_2$  by opening terminal A and B. Connect an ammeter between these terminals as shown in the figure-3. Now take the ammeter reading  $I$ , which is  $I_{\text{Norton}}$ .
3. Eliminate the voltage sources by shorting their terminals. Place an ohmmeter across terminal A and B as shown in the figure-4. Now take the ohmmeter reading which is  $R_{\text{Norton}}$ .
4. Now construct the Norton's equivalent circuit by adding  $I_{\text{Norton}}$  in parallel with  $R_{\text{Norton}}$ . Then connect load resistor  $R_2$  parallel to  $R_{\text{Norton}}$  between terminal A and B. The circuit should look like figure-5. Now take the ammeter reading  $I$ .

\*\*\*\*\*

**Lab Work: Experiment-6: Verification of Norton's Theorem**

\*\*\*\*\*

5. If the current reading of figure-2 is same as the reading found in figure-5, then Norton's theorem will be verified.
6. From the exact values of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $E_1$  and  $E_2$ , calculate  $I$  through  $R_2$  analytically. Compare the analytical value with that of the experimental value.

**5.7 Data Table:**

Fill up the following table and discuss on the experimental results.

Reading No.	I (mA) Fig-2	$I_{\text{Norton}}$ (mA)	$R_{\text{Norton}}$ (Ohm)	I (mA) Fig-5
1.				
2.				
3.				
4.				
5.				

**5.8 Result:**

Norton's Theorem has been verified.

\*\*\*\*\*